


Harshita N Kumar
ID: COMETFWC052

GATE Question No. 41

Question

For any set of inputs A and B , the following circuits give the same output Q , except one. Which one is it?

Given Circuits

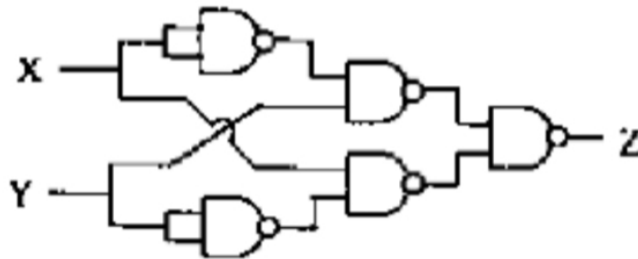

Question Analysis

Option (a):

$$Q = (A \oplus B)\overline{B}$$

Since $A \oplus B = A\overline{B} + \overline{A}B$,

$$Q = (A\overline{B} + \overline{A}B)\overline{B}$$

$$Q = A\overline{B}$$

Option (b):

$$Q = A\overline{B}$$

Option (c):

After simplification, it reduces to:

$$Q = A\overline{B}$$

Option (d):

$$Q = \overline{A} + B$$

Thus, option (d) produces a different output.

Truth Table Comparison

A	B	$A\overline{B}$	$\overline{A} + B$
0	0	0	1
0	1	0	1
1	0	1	0
1	1	0	1

Conclusion

Options (a), (b), and (c) implement the function:

$$Q = A\overline{B}$$

Option (d) implements:

$$Q = \overline{A} + B$$

Since the outputs are not identical for all input combinations, option (d) is the incorrect circuit.